

Units :

- 1] Introduction to electronics [15] mark
- 2] Transistors [10] marks
- 3] Operational Amplifiers [10] marks
- 4] Sensors . [10] marks
- 5] Number system and logic gates [20] marks

Co [Course outcome].

- 1] CO I → To understand the basics of Semiconductors and Components like diode, transistors and diode.
- 2] To introduce the fundamentals of electronic instruments and measurements

To implement logical operations on variables

Handwritten notes and diagrams on the bottom page of the notebook, including circuit symbols and logic diagrams.

Introduction to Electronics.

1] Introduction to electronics

2] Evolution of electronics

3] Active and passive components

A] Evolution of electronics

→ 1] E. of E have three key components, vacuum tube, transistor and IC's [Integrated circuits]

2] In 1883 → Thomas Edison addition → conductivity

3] 1904 - vacuum tube → Fleming

4] 1906 - W Lee - forest → develop vacuum triode.

5] 1927 → Macrone - invented radio

6] 1947 → John Bardeen → Transistor.

7] 1958 → First IC.

8] 1900 → vacuum tube [1st gen]

9] 1947 → 2nd gen

10] 1958, → 3rd gen

11] 1960 → SSI [Small Scale Integration]

- 12) 1966 → MSI
- 13) 1969 → LSI
- 14) 1975 → VLSI
- 15) 1995 → VLSI

Active and passive components.


Active and passive components

Active components can supply power in a electric circuit
 Eg generator, Transistor, Diode, Battery,


Passive Component → A passive component cannot deliver power
 it can only absorb power in their circuit
 Eg RLC [Resistance, Capacitance, inductor]

Active	Passive
Required external source for operation	Does not required external source.
Control flow of current	Cannot control flow of current.
Energy donor	Energy acceptor.
able to provide power gain	Not able to provide power gain.
Linear graph	Linear graph.
eg transistor, diode, Battery,	eg Inductor, Resistor, Capacitor.


Q1] PN-junction diode.

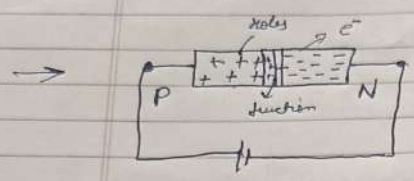

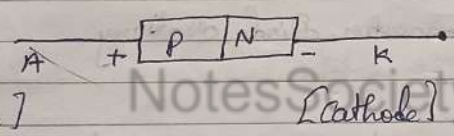
- 1] PN-junction diode it has two electrodes it is a semiconductor device having two terminals naming anode and cathode.
- 2] It allows currents to flow in one direction from its anode to cathode.



Symbol of diode.

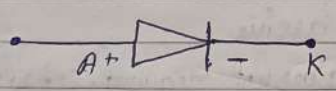

Zero Bias

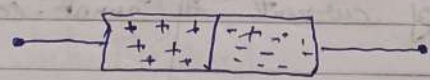

There is no connection of battery.
NO-Bias
It does not have any

a] Forward bias

→ 1] Positive terminal of battery is connected with positive terminal of the diode.

2] Negative terminal of battery is connected with negative terminal of diode.

3] When current flows in the diode the holes and depletion region become smaller.

4] It shows current moving in forward bias




b] Reverse bias

1] Positive terminal of battery is connected with negative terminal of the diode.


2] Negative terminal of battery is connected with positive terminal of the diode.

When current flows then the depletion region becomes larger.

It shows current moving in reverse bias

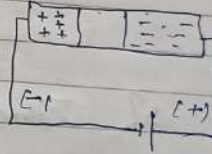


27 V-I characteristics of PN-junction.

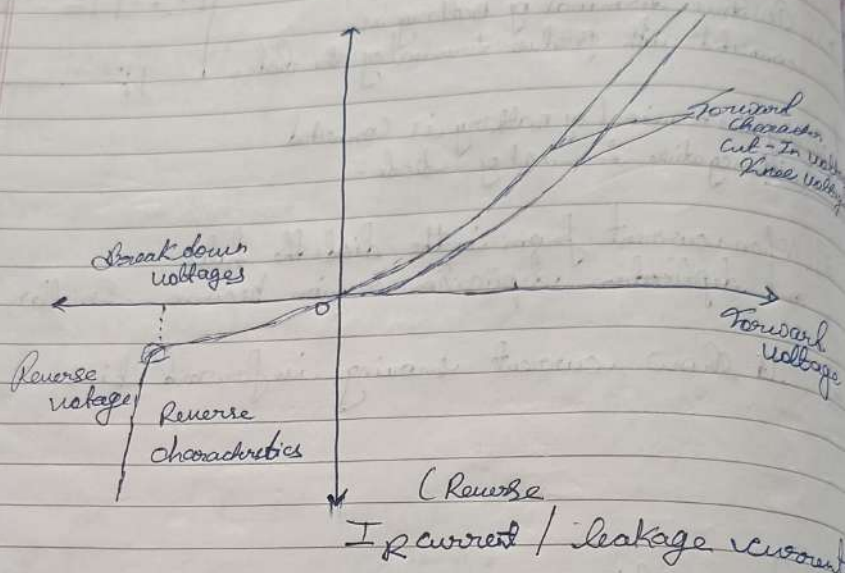


NotesSociety

37 Zener Diode.

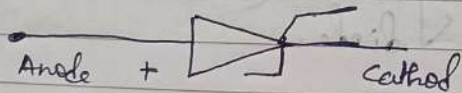


Symbiotic Representation of Zener Diode.

1]

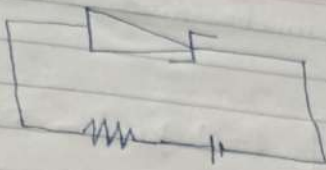


Zener Diode in forward bias.

2]


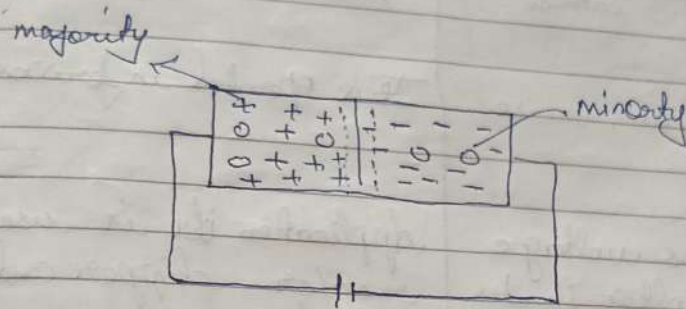


3]

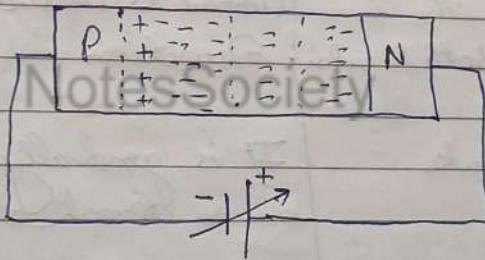


Reverse Bias Diode.

Difference Between PN-junction diode and Zener diode

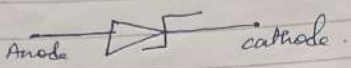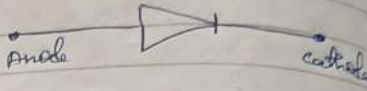Zener Diode	P-N junction Diode
1] 	
It is operated in reverse bias	It is operated in forward bias
2] It is used as voltage regulator, voltage limiter	Application it is used in rectifier, clipper and voltage multiplier.
1] In Zener Diode the current flow in both direction	Current is conducted in only one direction
It has sharp break down region.	It is gradually increasing reverse break down.
	V-I characteristic of Zener Diode

V-I characteristics of Z.D.

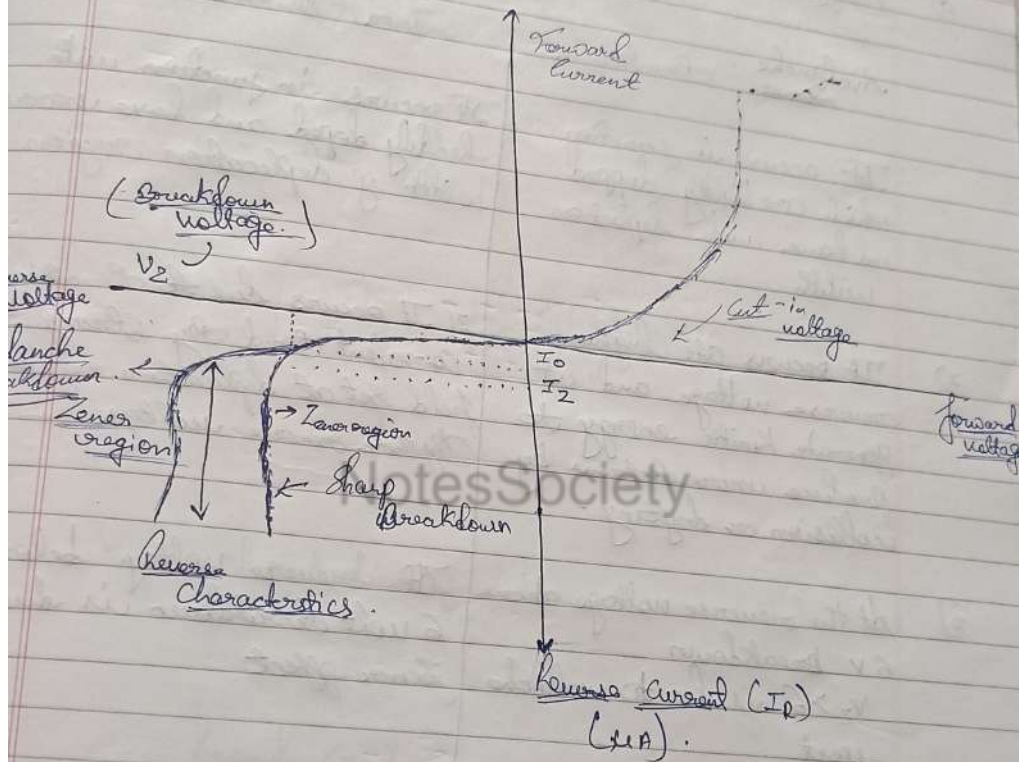

Zener Breakdown \rightarrow at small level.

Avalanche Breakdown \rightarrow at large current.

① Difference Between Avalanche Breakdown and Zener Breakdown

Avalanche Breakdown	Zener Breakdown
It occurs in junction which are lightly doped and have wide depletion width	It occurs in junction with heavily doped and have narrow width of depletion region.
It occurs at higher reverse voltage and it generate kinetic energy to produce more electrons by collision or drifting.	It occurs due to breaking of co-valent bond by strong electric field set at depletion region by these reverse voltage.
At the reverse voltage above 6V breakdown $V_Z > 6$ is due to avalanche effect	At reverse voltage below 6 volt breakdown is due to Zener effect
Electric field produce is less or weak in nature	At reverse voltage strong electric field is produce
Charge carriers obtain energy on the applied voltage	Zener current is independent of applied voltage.

① Difference Between Avalanche Breakdown and Zener Breakdown

Avalanche Breakdown

It occurs in junction which are lightly doped and have wide depletion width.

2) It occurs at higher reverse voltage and it generate kinetic energy to produce more electrons by collision or drifting.

3) At the reverse voltage above 6V breakdown $V_Z > 6$ is due to avalanche effect.

Electric field produce is less or weak in nature.

Charge carrier obtain energy from the applied voltage.

Zener Breakdown

It occurs in junction with heavily doped and have narrow width of depletion region.

2) It occurs due to breaking of covalent bond by strong field set at depletion region by these reverse voltage.



3) It reverse voltage below 6 volt Breakdown is due Zener effect.

At reverse voltage strong electric field is produce.

Zener current is independent applied voltage.


Led [Light Emitting diode]

Symbol of LED

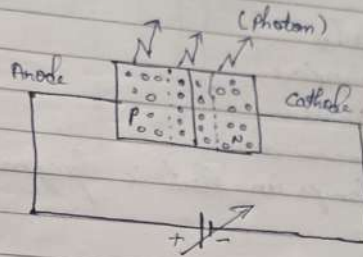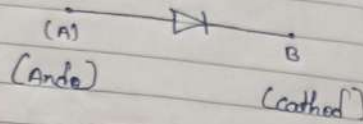

V-I characteristics of Led.

NotesSociety

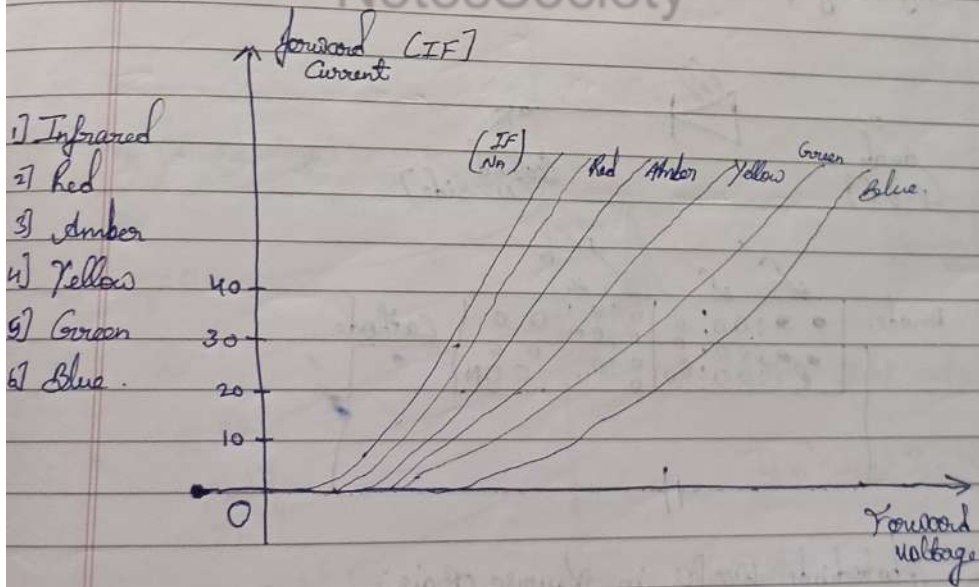



It work on principle electroluminescence which converts electrical energy into light energy.

Application of LED.

- 1] LED.
- 2] Camera Flashes.
- 3] Digital Computers.
- 4] Traffic Signals.
- 5] Optical Communication.
- 6] Indicator lamps in Electric Equipments.


* Photodiode

Symbol of photodiode.

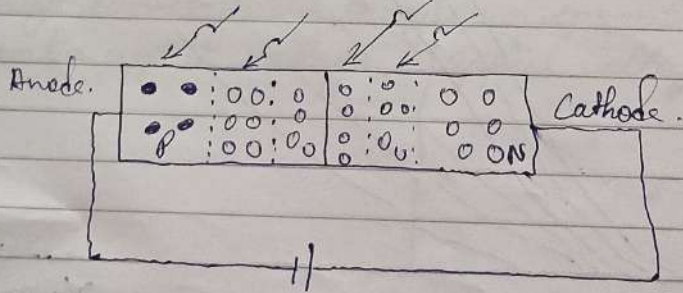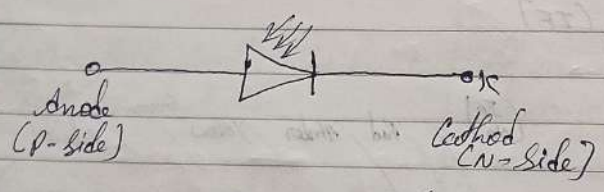


Photodiode works in Reverse Bias.

V-I characteristics of photo-Diode.

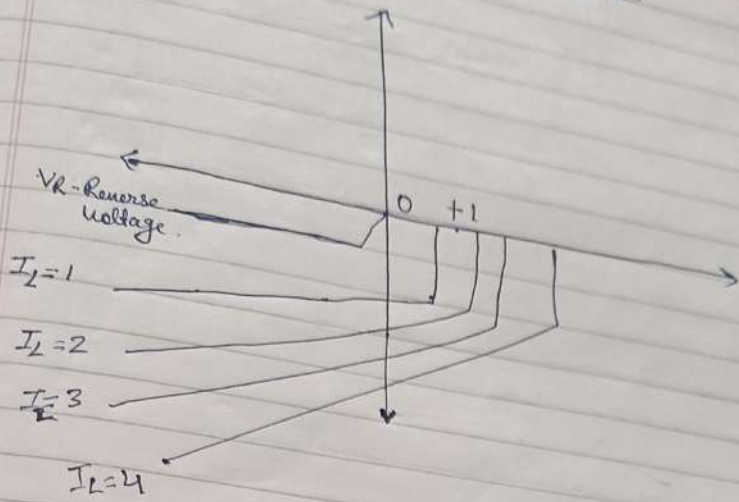


NotesSociety

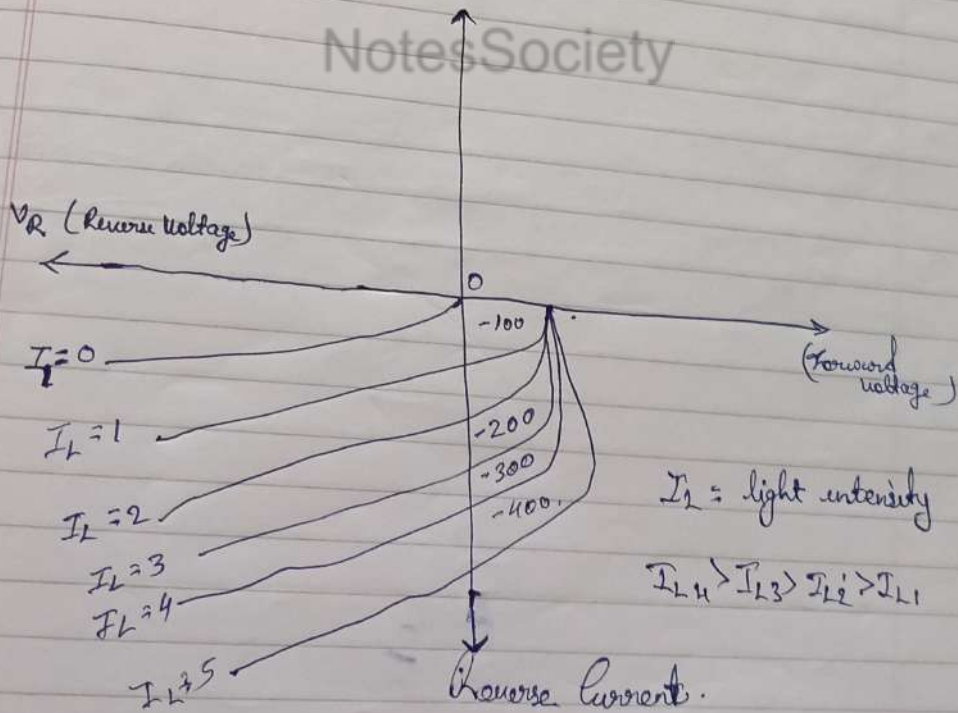

Step

Bridge Rectifier

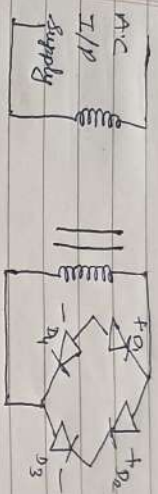


When two half cycle

$D_1 D_4 \rightarrow F.B.$
 $D_2 D_3 \rightarrow R.B.$


When -ve half cycle.

$D_1 D_3 - F.B.$
 $D_2 D_4 - R.B.$

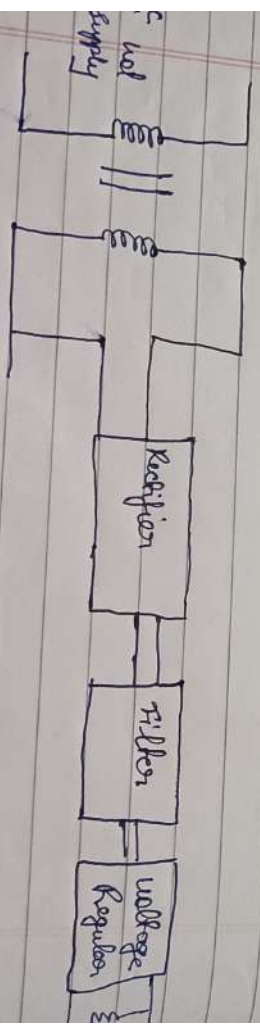Block diagram of DC Regulated power supply.



Steady State DC Regulated Power Supply.

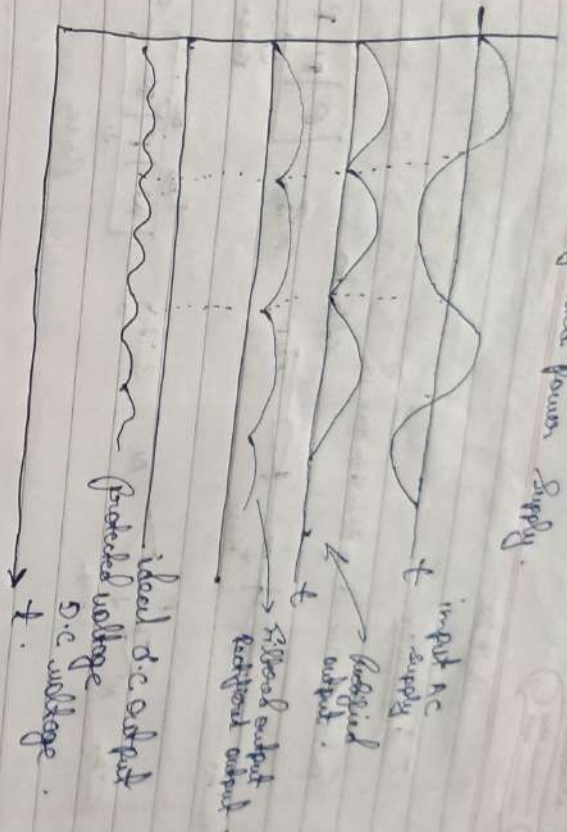


NotesSociety

Unit III

Transistor

Equivalent circuit of transistor are.

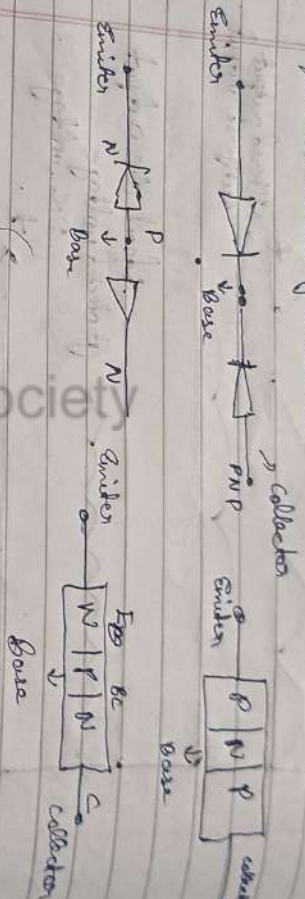

→

Transistor are 3 terminal device the terminals are emitter, base, collector. It is current controlled device. The types of transistor are.


a] $\text{PNP} \rightarrow \text{Transistor}$

b] $\text{NPN} \rightarrow \text{Transistor}$

3] Equivalent transistor.

Operation of N-P-N transistor.

Structure:

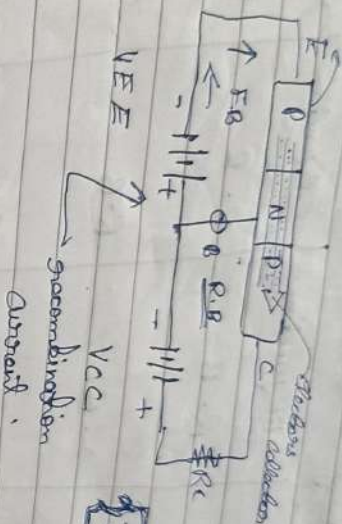

$$I_E = I_C + I_B$$


→ ① Electrons are majority carriers

② E. injected & collected at collector

③ Recombination.

Operation of P-N-P transistor.

Structure/Emitter

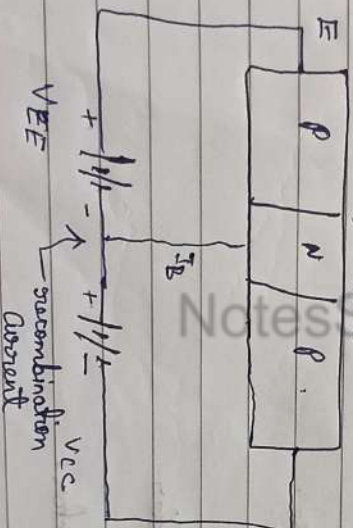

Regions of transistor

Regions of Transition


Region	BE function	CE function	Application
1] Cut-off region	R.B	R.B	Class open switch
2] Active region	F.B	R.B	Amplifier
3] Saturation Region	F.B	F.B	Class switch

Configuration of transistor

CE - Common Base


CF - Common emitter

CC - Common collector

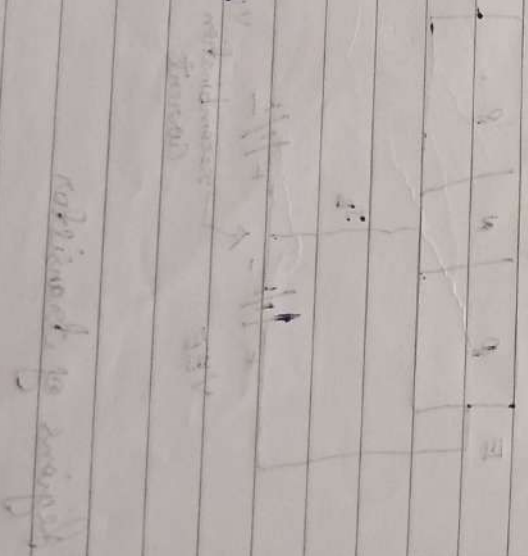


Robinson to bridge

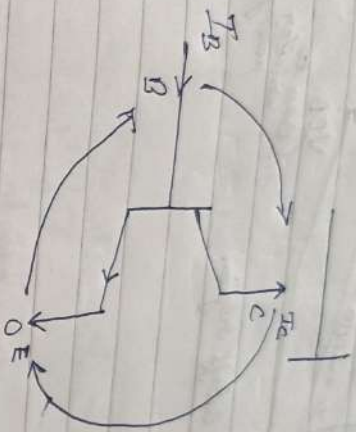
- 1] Draw block diagram of D.C. Supply from supply
- 2] Explain working principle of n-p-n transistor
- 3] Explain working principle of p-n-p transistor.



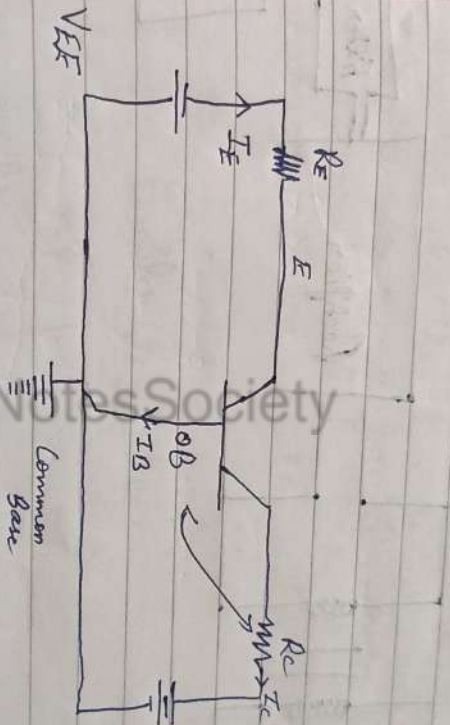- 1] I_E
- 2] I_B
- 3] I_C
- 4] V_{CE}
- 5] V_{BE}
- 6] V_{BC}



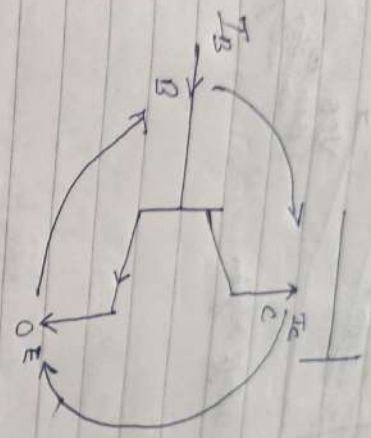
- 1] Draw circuit diagram of D.C. Supply from battery
- 2] Explain working principle of n-p-n transistor.
- 3] Explain working principle of p-n-p transistor.




- 1] I_E
- 2] I_B
- 3] I_C
- 4] V_{CE}
- 5] V_{BE}
- 6] V_{BC}



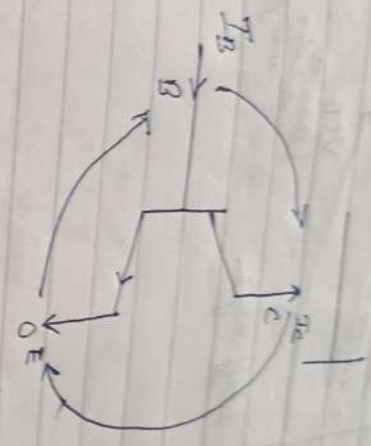Q Explain working principle of n-p-n transistor.
 Explain working principle of p-n-p transistor.



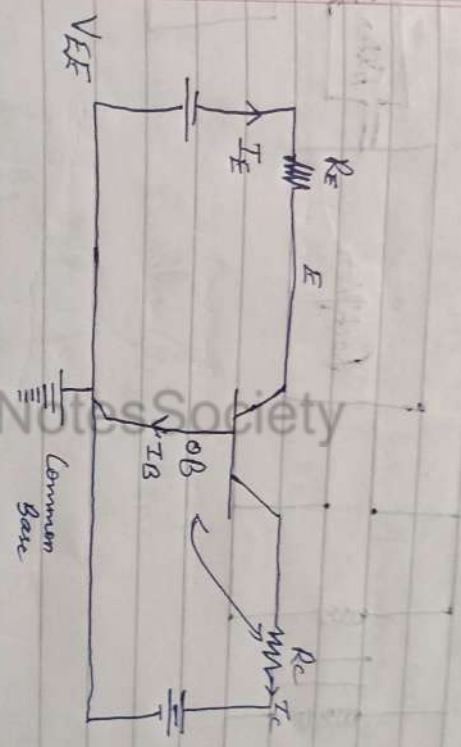- 1] I_E
- 2] I_B
- 3] I_C
- 4] V_{CE}
- 5] V_{BE}
- 6] V_{BC}






Configuration of transistors.

- 1) Common Base
- 2) Common Emitter
- 3) Common Collector

* Common Base Configuration where base terminal is common to input and output.
 The input is applied between emitter and base terminal where V_{BE} and I_{BE} are the parameters. Output is taken across base and collector terminal $\alpha =$ current amplification factor where α is the ratio of collector current to emitter current.

Common Emitter Configuration.

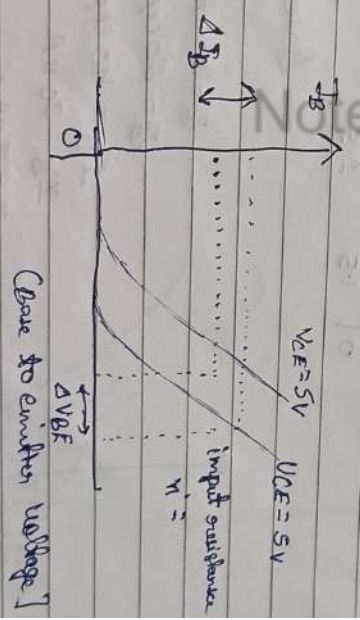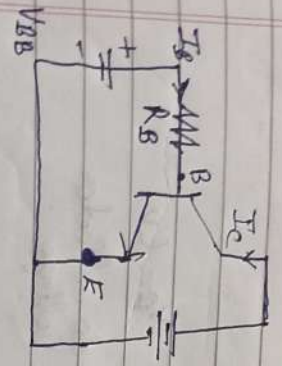


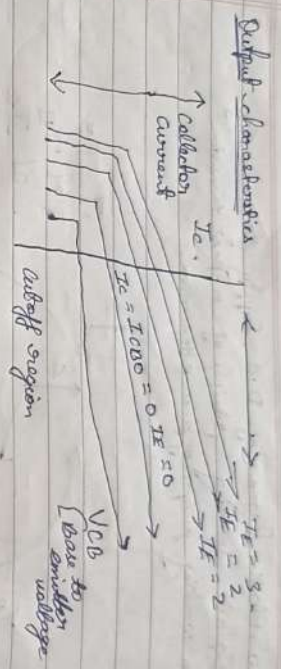


Q

Input


AC in not supply

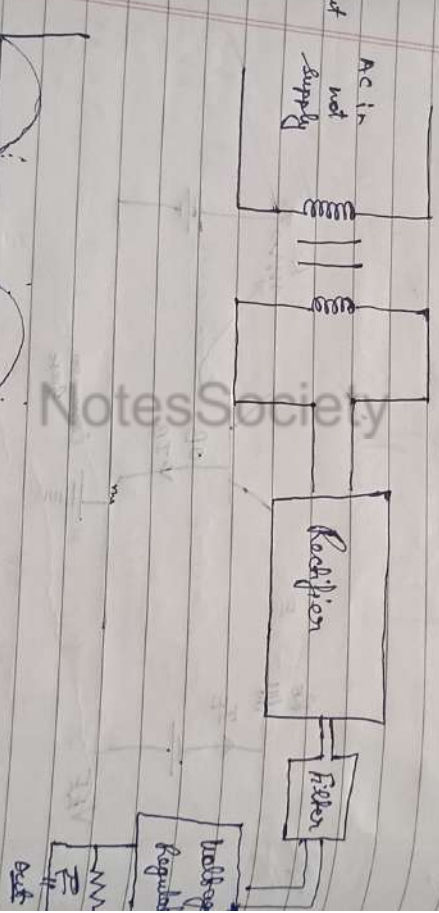


Q

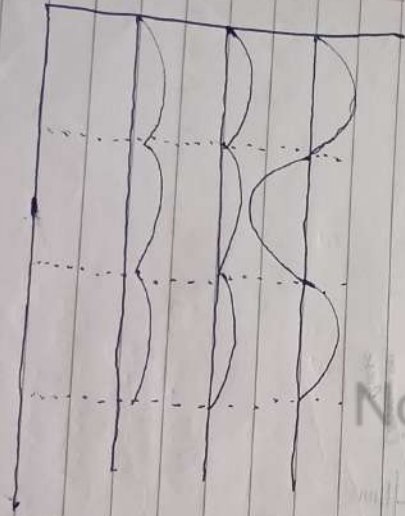

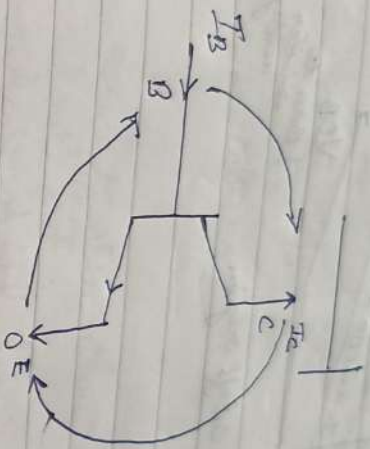- Q] Draw circuit diagram of D.C. Supply for biasing of n-p-n transistor.
- Q] Explain working principle of p-n-p transistor.



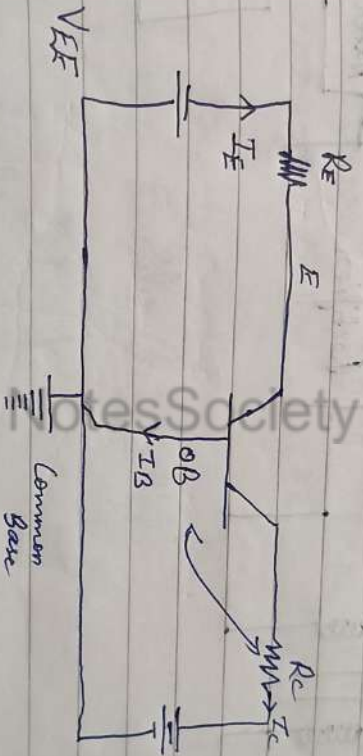- 1] I_E
- 2] I_B
- 3] I_C
- 4] V_{CE}
- 5] V_{BE}
- 6] V_{BC}
- 7] V_{E}



Configuration of transistor

Common collector configuration



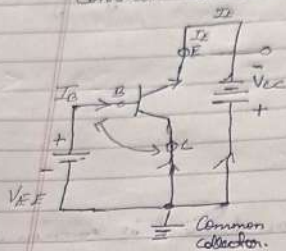


Fig Common Collector Configuration of NPN transistor
or Emitter follower

Input character...

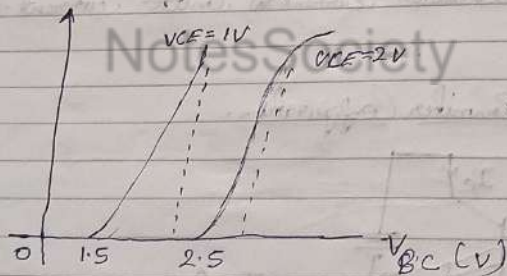

Base to collector voltage

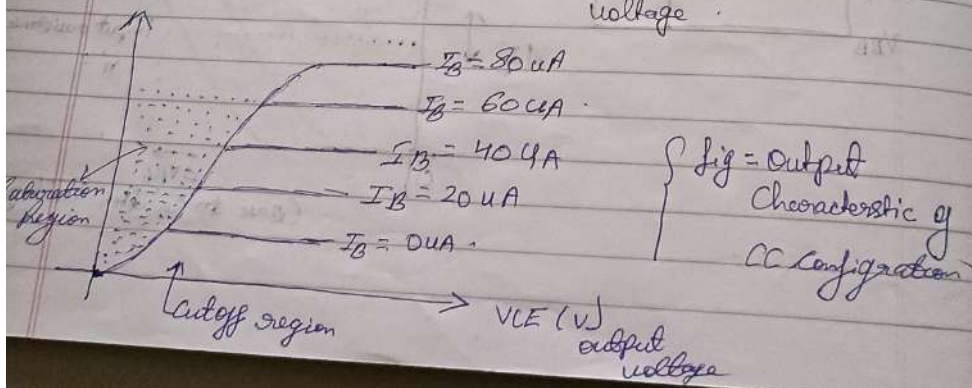

} Fig = Output characteristic of CC configuration





C- Configuration Application:

- 1] It is used as audio-amplifier
- 2] used in power amplifiers
- 3] transistor is used as switch as well
- 4]





Application of CC Configuration

- It is used in switching circuit.





CB

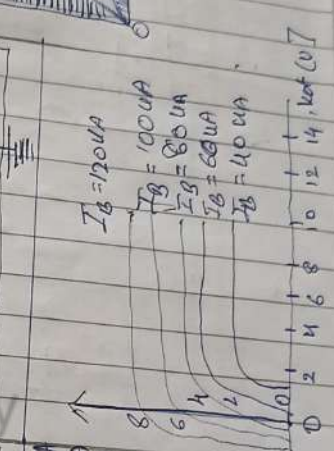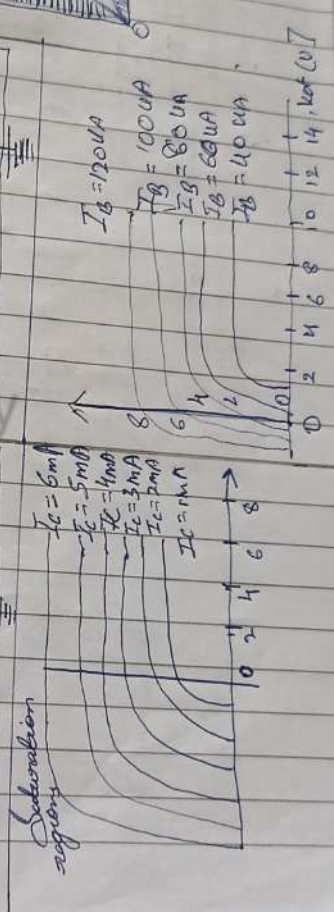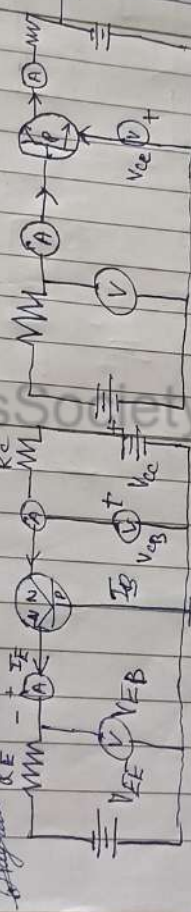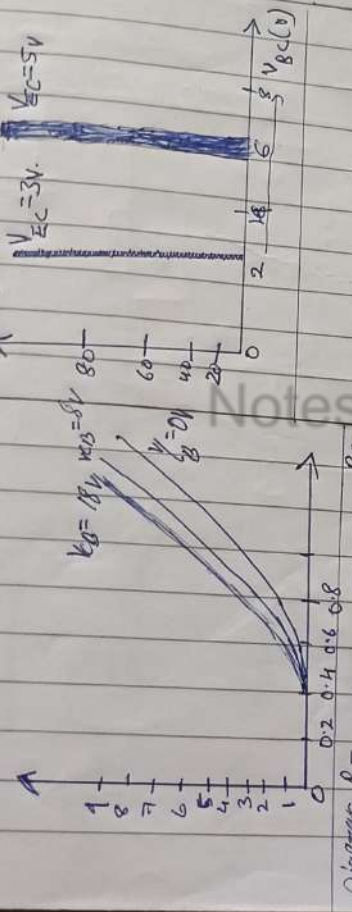

CE

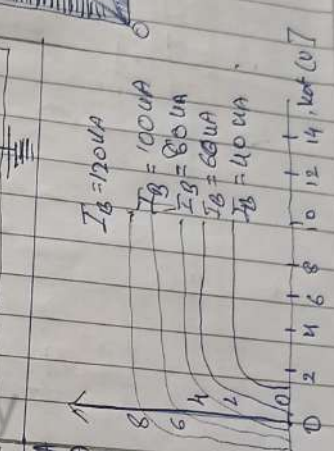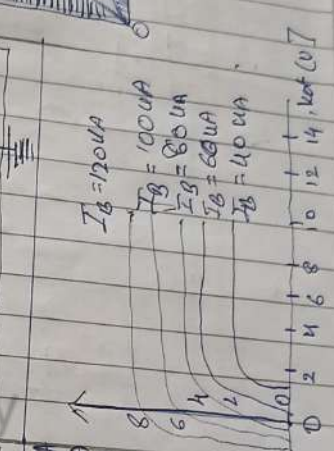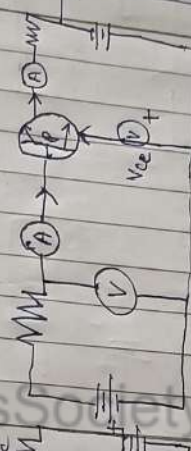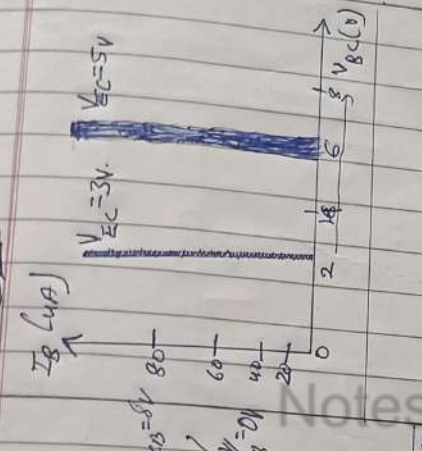


CE

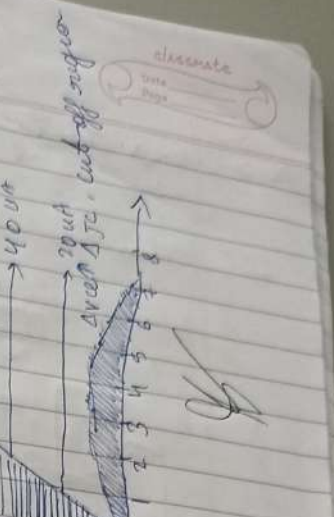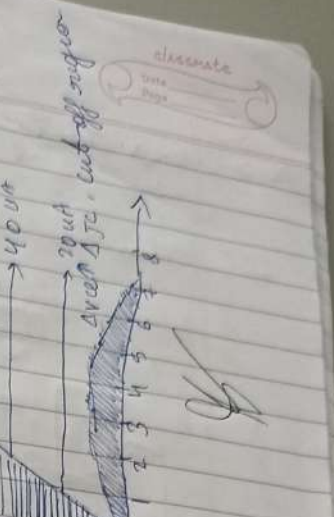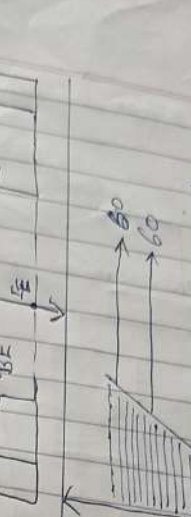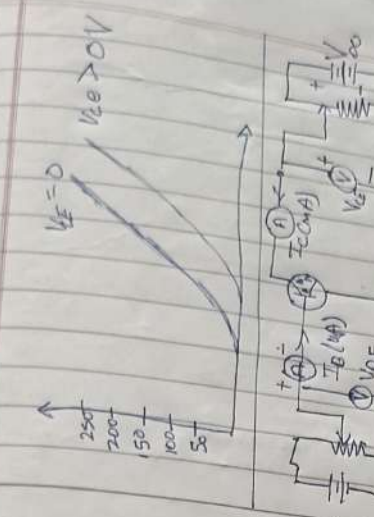

classmate
Date
Page

Parameters Difference Between CB, CE, CC configuration of transistor.

Parameters	Common Base	Common Emitter	Common collector
Input Terminal	Emitter	Base	Emitter
Output Terminal	Collector	Collector	Collector
Voltage Gain	Low	Moderate	Slightly less than unity gain
Current Gain	Medium	High	Low current gain (Current Shifting)
Power gain	Low to moderate	Moderate to High	NO (Depends on β or 360 degree)
Phase inversion	NO (Degree or 360 degree)	Yes (180 degree)	Yes (360 degree)
Input Impedance	Low (50 ohm)	Moderate	High (300 k ohm)
Output Impedance	High (1 m ohm)	Moderate	Low (300 ohm)
Applications	High frequency amplifiers RF circuits	General purpose amplifiers Power amplifiers	Voltage buffering Matching

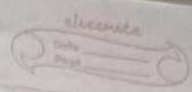

Difference VJT transistor and Fet .

VJT	FET
→ 1) Three terminal device	3 terminal device have drain and gate terminal.
→ 2) It is used as analog control device	It is voltage control device
3) It is use as high log switching application	It is used as high switching application.
4) It is use as Bipole device used as amplifier	It is used as power
5) It has high gain	It has low gain.

Difference VJT transistor and Fet.

VJT	FET
→ 1) Three terminal device	3 terminal device have drain and gate terminal.
→ 2) It is used as current control device	It is voltage control device
3) It is use as high log switching application	It is used as high switching application.
4) It is use as Bipole device used as amplifier	It is used as power
5) It has high gain	It has low gain.



classmate
Date _____
Page _____

Difference VJT Transistor and Fet .

VJT	FET
→ 1) Three terminal device	3 terminal device have drain and gate terminal.
→ 2) It is used as current control device	It is voltage control device
3) It is use as high log switching application	It is used as high switching application .
4) It is use as Bipole device used as amplifier	It is used as power o
5) It has high gain	It has low gain .

→ N-channel JFET construction:

□ When

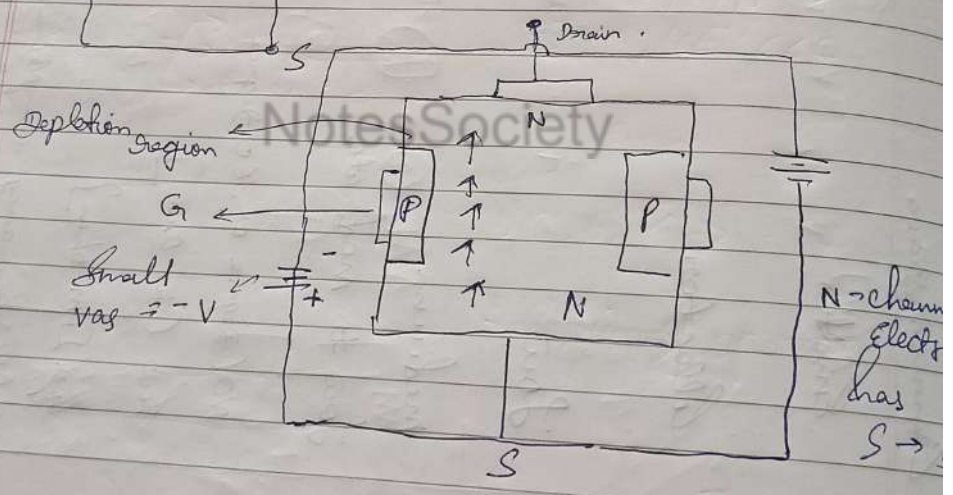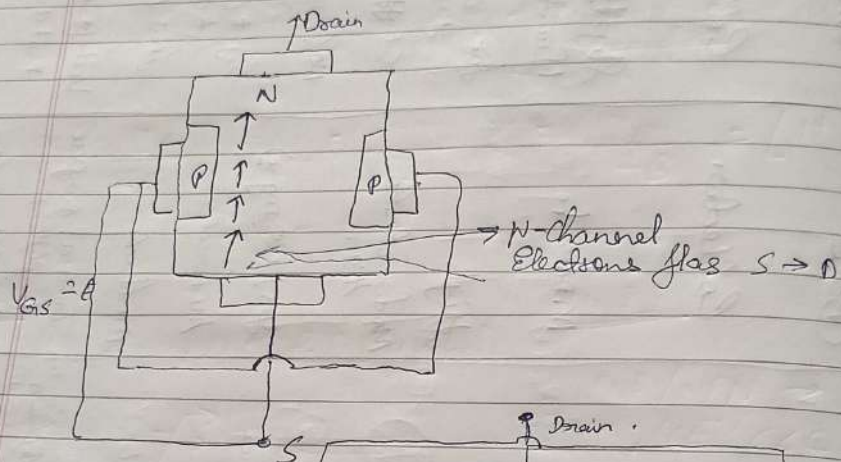

① Small voltage is applied.

classmate
Date _____
Page _____

Difference VJT transistor and Fet .

VJT	FET
→ 1) Three terminal device	3 terminal device have drain and gate terminal.
→ 2) It is used as current control device	It is voltage control device
3) It is use as high leg switching application	It is used as high switching application.
4) It is use as Bipole device used as amplifier	It is used as power
5) It has high gain	It has low gain .

Notes Society

Q.1) Difference VJT characteristic and Fet .

VJT

- 1) Three terminal device
- 2) It is used as control device
- 3) It is use as high log switching application
- 4) It is use as Bipole device used as amplifier
- It has high gain

FET

- 3 terminal device have drain source and gate terminal.
- It is voltage control device.
- It is used as high switching application.
- It is used as power amplification.
- It has less gain.

Difference VJT transistor and Fet .

VJT	FET
→ 1) Three terminal device	3 terminal device have drain and gate terminal.
→ 2) It is used as current control device	It is voltage control device
3) It is use as high log switching application	It is used as high switching application .
4) It is use as Bipole device used as amplifier	It is used as power o
5) It has high gain	It has low gain .

CB	CE	CC
α	β	γ
Alpha	Beta	Gamma

} Current region

$$\alpha = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_c}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit II

N, Zener, LED, P.D Symbols

Wien $\begin{cases} \rightarrow \text{HWR} \\ \rightarrow \text{FWR} \\ \rightarrow \text{Bridge} \end{cases}$

Power supply

- 1] PNP/NPN \rightarrow Equivalent
- 2] CB, CE, CC

3] Difference

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operation

Difference VJT transistor and Fet .

VJT

- 1) Three terminal device
- 2) It is used as ~~control~~ control device
- 3) It is use as high log switching application
- 4) It is use as Bipole device used as amplifier

It has high gain

FET

- 3 terminal device have drain source and gate terminal.
- It is voltage control device.

It is used as high switching application.

It is used as power amplification

It has less gain .

Difference VJT transistor and Fet.

VJT

- 1) Three terminal device
- 2) It is used as ~~control~~ control device
- 3) It is use as high log switching application
- 4) It is use as Bipole source used as amplifier

It has high gain

FET

- 3 terminal device have drain source and gate terminal.
- It is voltage control device.

It is used as high switching application.

It is used as power amplification.

It has less gain.

CB CE CC
 α β γ
 Alpha Beta Gamma.

} Current region

$$\alpha = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit II

N, Zener, LED, P-D Symbols

Amplifier $\begin{cases} \rightarrow$ HWR
 \rightarrow FWR
 \rightarrow Bridge.

Power Supply

- 1] PNP/NPN \rightarrow Equivator
- 2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators.

CB	CE	CC
α	β	γ
Alpha	Beta	Gamma

} Current Gain

$$\alpha = \frac{I_C}{I_E} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit II

Diodes, Zener, LED, P.D. symbols

Amplifier \rightarrow High
 \rightarrow Freq R
 \rightarrow Bridge.

Power supply

Notes: PNP/NPN \rightarrow Equivalents

2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operation.

CB CE CC
 α β γ
 Alpha Beta Gamma

Current
~~Equation~~

$$\alpha = \frac{I_E}{I_B} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

P.N., Zeros, P.O., P.D. Symbols
 Transfer f_z, f_p
 La Bridge

Notes Society / FN → Equations

1) CB, CE, CC

2) Difference

3) α, β, γ → solution

4) Region of operation

Power Supply

CB CE CC

α β γ

Alpha Beta Gamma

} Current
region

$$\alpha_{dc} = \frac{I_C}{I_E} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

✓ PN, Zener, LED, P-D Symbols

✓ Rectifier \rightarrow HCR
 \rightarrow FCR
 \rightarrow Bridge.

Power supply

Unit II

✓ PNP/NPN \rightarrow Equivalents
✓ CB, CE, CC

3) Difference.

4) $\alpha, \beta, \gamma \rightarrow$ relation

5) Region of operation.

CB CE CC
 α β γ
 Hpa Cbda Gava.

} Current
Supply

$$\frac{\alpha}{\beta} = \frac{I_C}{I_E} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta)_{dc}$$

Unit II

PM, Zener, LED, P.D. Symbols

Notes on PNP/PPN → Equiv. Circ

Rectifier → HIGH
 → Fwd B.
 → Bridge.

2] CB, CE, CC

3] Difference.

Power Supply

4] α, β, γ → relation

5] Region of operation.

CB	CE	CC
α	β	γ
Alpha	Beta	Gamma

} Current
Supply

$$\alpha = \frac{I_E}{I_B} \quad \beta_{CC} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta) \alpha$$

Part I
PA, Zener, LED, P.D. Symbols

Part II

Rectifier \rightarrow ^{PIEC} Full
 \rightarrow Bridge

Notes Society / PN \rightarrow Equations

1) CB, CE, CC

Power Supply

3) Difference

4) $\alpha, \beta, \gamma \rightarrow$ relation

5) Region of operation

CB	CE	CC
α	β	γ
Alpha	Beta	Gamma

} Current region

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta)_{dc}$$

Unit I

- 1) PN, Zener, LED, P-D Symbols
- 2) Rectifier $\begin{cases} \rightarrow HWR \\ \rightarrow FWR \\ \rightarrow Bridge \end{cases}$

Power supply

Unit II

- 1) PNP/NPN \rightarrow Equivale
- 2) CB, CE, CC
- 3) Difference
- 4) $\alpha, \beta, \gamma \rightarrow$ relation
- 5) Region of operators

CB	CE	CC
α	β	γ
Alpha	Beta	Gamma.

} Current
Region

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_c}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta)_{dc}$$

Unit I

1] PN, Zener, LED, P.D Symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

Power Supply

Unit II

1] PNP/NPN \rightarrow Equivalents

2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators.

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha = \frac{I_E}{I_F} \quad A_{dc} = \frac{I_c}{I_b} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta)_{dc}$$

Unit I

1) PN, Zener, LED, P-D Symbols

2) Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge

Power supply

Unit II

1) PNP/NPN \rightarrow Equivalents
 2) CB, CE, CC

3) Difference

4) $\alpha, \beta, \gamma \rightarrow$ relation

5) Region of operation

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma.	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P.D Symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

3] Power supply

Unit II

1] PNP/NPN \rightarrow Equivalent

2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operation.

CB	CE	CC	} <u>Current</u> <u>gains</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

- 1] PN, Zener, LED, P-D Symbols
- 2] Rectifier $\begin{cases} \rightarrow \text{HW R} \\ \rightarrow \text{FW R} \\ \rightarrow \text{Bridge} \end{cases}$
- Power supply

Unit II

- 1] PNP / NPN \rightarrow Equivale
- 2] CB, CE, CC
- 3] Difference.
- 4] $\alpha, \beta, \gamma \rightarrow$ relation
- 5] Region of operators.

CB	CE	CC	} <u>Circuit</u> <u>regions</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

- 1] PN, Zener, LED, P.D symbols
- 2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.
- 3] Power supply

Unit II

- 1] PNP/NPN \rightarrow Equival
- 2] CB, CE, CC
- 3] Difference.
- 4] $\alpha, \beta, \gamma \rightarrow$ relation
- 5] Region of operators.

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

- 1) PN, Zener, LED, P-D Symbols
- 2) Rectifier $\begin{cases} \rightarrow \text{HWR} \\ \rightarrow \text{FWR} \\ \rightarrow \text{Bridge} \end{cases}$
- 3) Power supply

Unit II

- 1) PNP/NPN \rightarrow Equivale
- 2) CB, CE, CC
- 3) Difference
- 4) $\alpha, \beta, \gamma \rightarrow$ relation
- 5) Region of operators

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P-D Symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

3] Power Supply

Unit II

1] PNP/NPN \rightarrow Equivalent

2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operation.

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma.	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P.D Symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

3] Power supply

Unit II

1] PNP/NPN \rightarrow Equivalent

2] CB, CE, CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators.

CB	CE	CC	} <u>Current</u> <u>gains</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P.D. symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow bridge.

Power Supply

Unit II

1] PNP/NPN \rightarrow Equations

2] CB, CE/CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators.

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{dc} = \frac{I_C}{I_E} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P-D symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

Power supply

Unit II

1] PNP/NPN \rightarrow Equations

2] CB / CE / CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operation.

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma.	

$$\alpha_{cc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_c}{I_b} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

- 1] PN, Zener, LED, P.D Symbols
- 2] Rectifier $\begin{cases} \rightarrow HWR \\ \rightarrow FWR \\ \rightarrow Bridge. \end{cases}$
- 3] Power supply

Unit II

- 1] PNP / NPN \rightarrow Equivale
- 2] CB, CE, CC
- 3] Difference.
- 4] $\alpha, \beta, \gamma \rightarrow$ relation
- 5] Region of operators.

classmate
Date _____
Page _____

Current Amplification factor (γ)

$$\gamma = \frac{\Delta I_C}{\Delta I_B} = \frac{\text{Output Current}}{\text{Input Current}}$$

Relation between γ & α

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \text{--- (1)} \quad \gamma = \frac{\Delta I_C}{I_B} \quad \text{--- (2)}$$

As we know $\Delta I_E = \Delta I_C + \Delta I_B$

$$\therefore \Delta I_B = \Delta I_E - \Delta I_C$$

$$\gamma = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} \quad \left\{ \text{Put Value of } \Delta I_B \text{ in } \gamma \right\}$$

Now

~~N.B.~~ ~~N.B.~~ N.B. of by ΔI_E

$$\gamma = \frac{\Delta I_C / \Delta I_E}{\Delta I_E / \Delta I_E - \Delta I_C / \Delta I_E}$$

$$\gamma = \frac{1}{1 - \alpha}$$

CB	CE	CC	} <u>Current region</u>
α	β	γ	
Alpha	Beta	Gamma	

$$\alpha_{cc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_c}{I_B} \quad \gamma = \frac{I_E}{I_B} = [1 + \beta_{dc}]$$

Unit I

1] PN, Zener, LED, P.D symbols

2] Rectifier $\begin{cases} \rightarrow HWR \\ \rightarrow FWR \\ \rightarrow Bridge. \end{cases}$

Power supply

Unit II

1] PNP/NPN \rightarrow Equivalent

2] CB, CE, CC

3] Difference

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators

CB	CE	CC	} <u>current region</u>
α	β	γ	
Alpha	Beta	Gamma.	

$$\alpha_{dc} = \frac{I_E}{I_F} \quad \beta_{dc} = \frac{I_C}{I_B} \quad \gamma = \frac{I_E}{I_B} = (1 + \beta_{dc})$$

Unit I

1] PN, Zener, LED, P.D Symbols

2] Rectifier \rightarrow HWR
 \rightarrow FWR
 \rightarrow Bridge.

Power supply

Unit II

1] PNP / NPN \rightarrow Equivale

2] CB, CE / CC

3] Difference.

4] $\alpha, \beta, \gamma \rightarrow$ relation

5] Region of operators.

For Common emitter Configurations -

$$\alpha = \frac{I_c}{I_E} \quad \left\{ \begin{array}{l} I_c = \text{Collector - Current} \\ I_E = \text{Emitter - Current} \end{array} \right.$$

$$\text{and } \beta = \frac{I_c}{I_B} \quad \left\{ \begin{array}{l} I_B = \text{Base - Current} \end{array} \right.$$

Also relation b/w I_c , I_B & I_E is

$$I_E = I_B + I_c$$

So

$$\alpha = \frac{I_c}{I_c + I_B}$$

$$\frac{1}{\alpha} = 1 + \frac{I_B}{I_c}$$

$$\frac{1}{\alpha} = 1 + \frac{I_B}{I_c}$$

$$\boxed{\frac{1}{\alpha} = 1 + \frac{1}{\beta}}$$


$$\boxed{\alpha = \frac{\beta}{1 + \beta}}$$

$$\left\{ \beta = \frac{I_c}{I_B} \right.$$

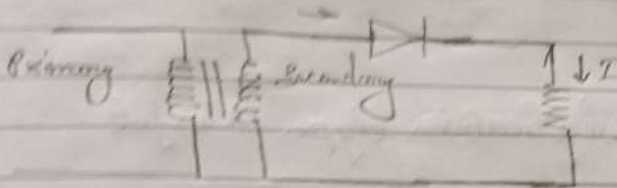Q11

Which rectifier will conduct for half cycle? Draw the construction and explain it with transformer.

→ A half wave rectifier is a type of rectifier which converts the positive half cycle of the input signal pulsating DC output signal.




2] The AC source supplies alternating current to the circuit. The alternating current is often represented by a sinusoidal waveform.


3] The step-down transformer reduces the AC voltage from high to low. In half rectifier we generally use a step-down transformer because the voltage needed for the diode is very small. Applying a large AC voltage without using transformer will permanently destroy the diode. So we use step-down transformer in half wave rectifier.


4] A diode is a two terminal that allows electric current in one direction in one direction and blocks

Classification of MOSFET.

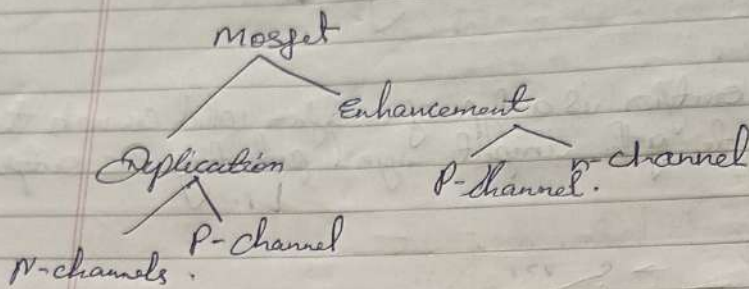


P-n-channel depletion type MOSFET

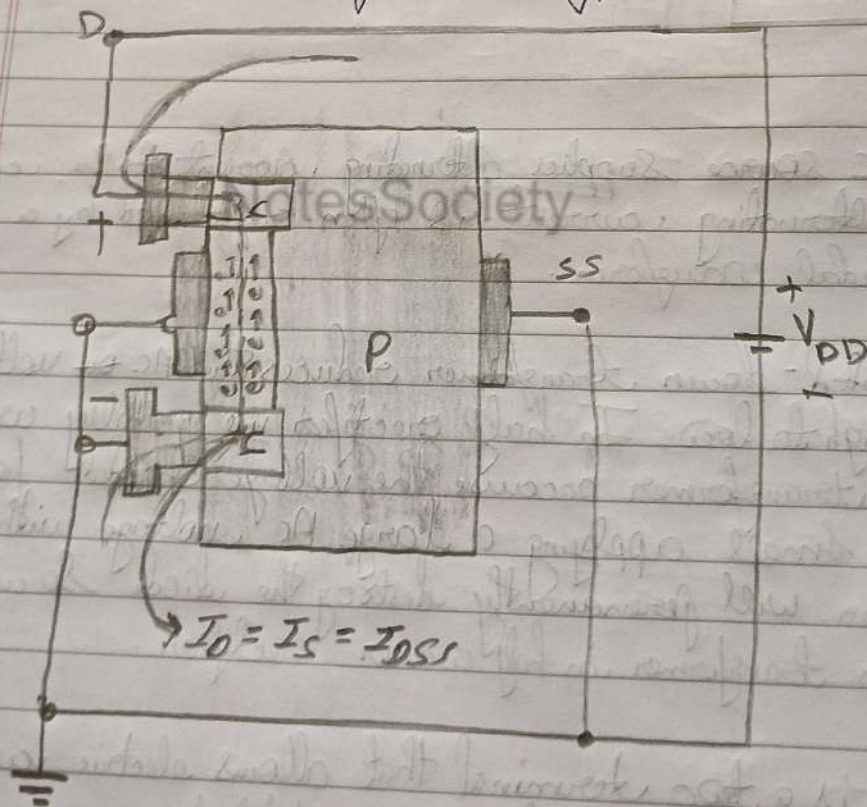


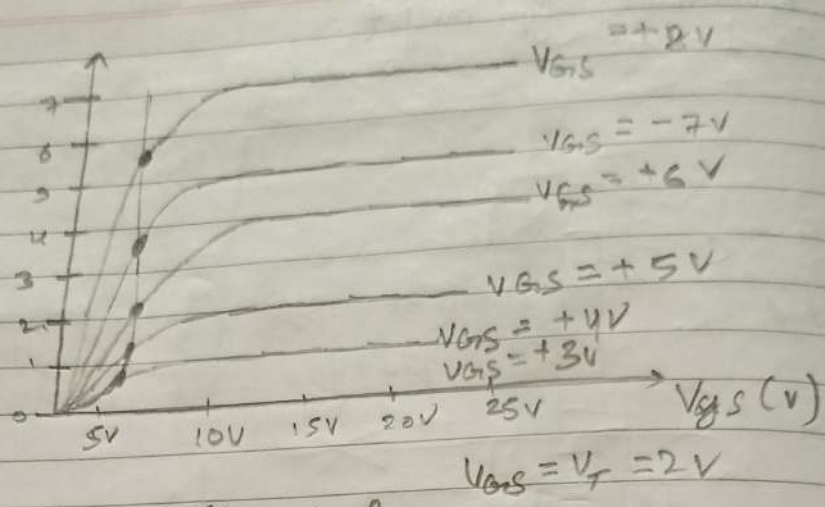


Drain Characteristics -

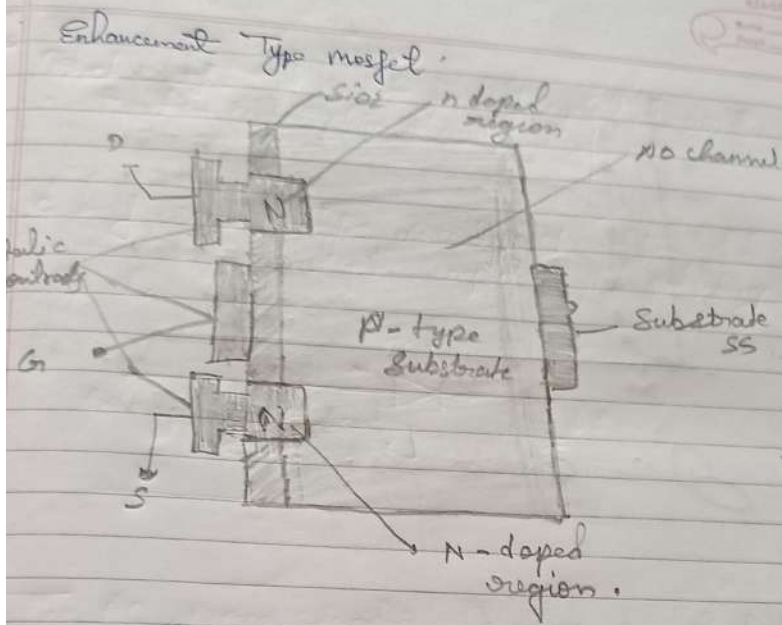

Transfer Characteristics

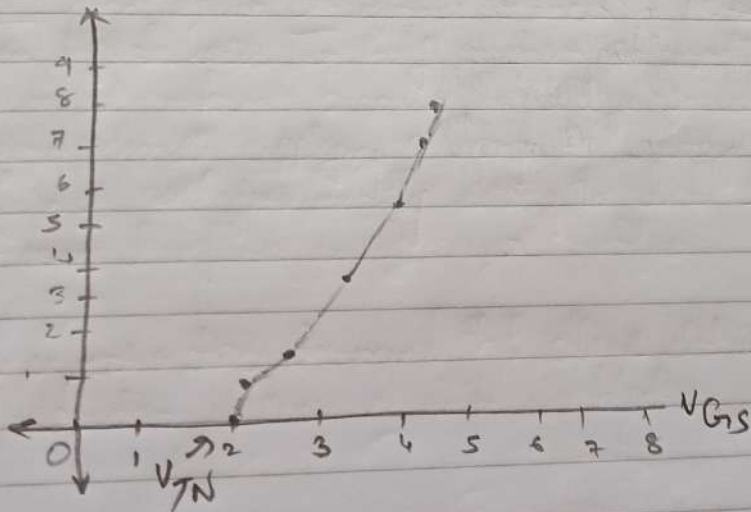


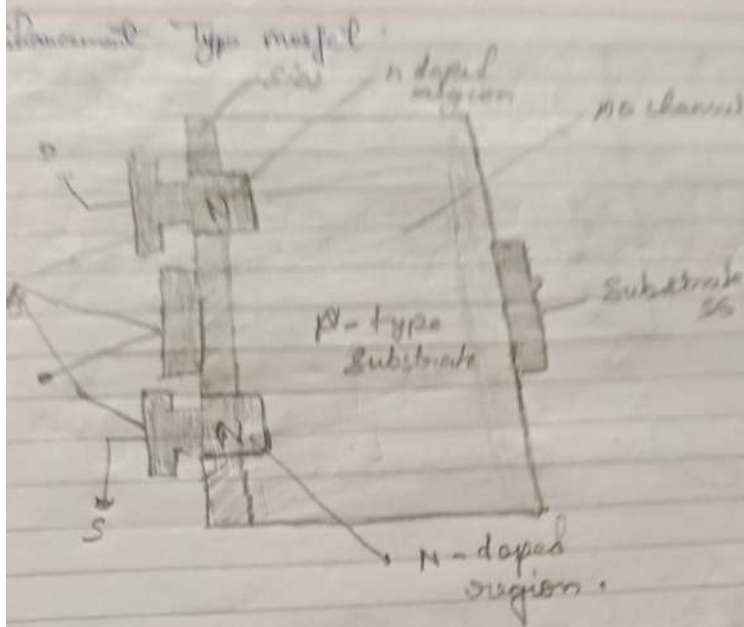Transfer characteristic of an n-channel Enhancement mosfet



NotesSociety

Transfer Characteristics

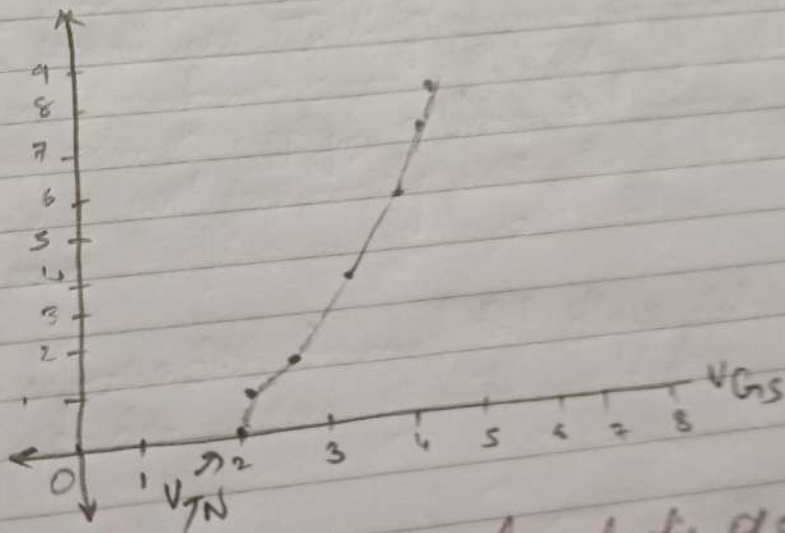


Transfer characteristic of an n-channel enhancement mosfet


Operational Amplifier:

1] Operational Amplifier: Is a integrated circuit which is used perform linear, non-linear mathematical operations.

Construction of operational amplifier.

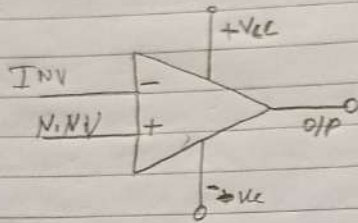


Structure of IC 741

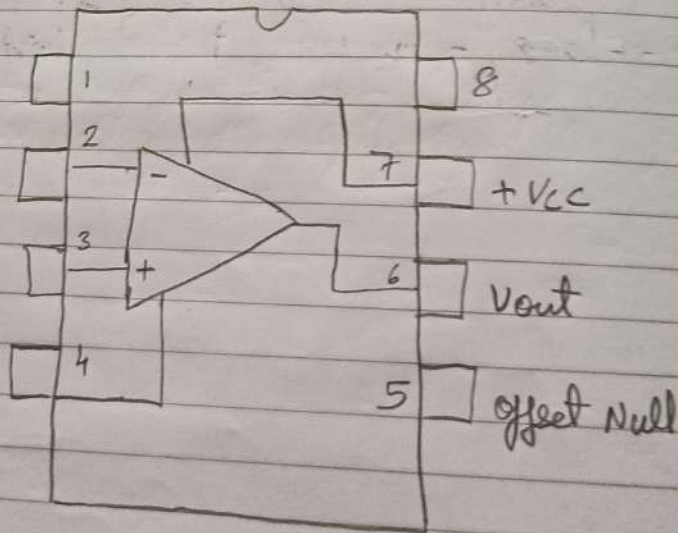

- 17 Pin 1: Offset Null
- 27
- 3)
- 4)
- 5)
- 6)
- 7)
- 8)

Block diagram of operational A

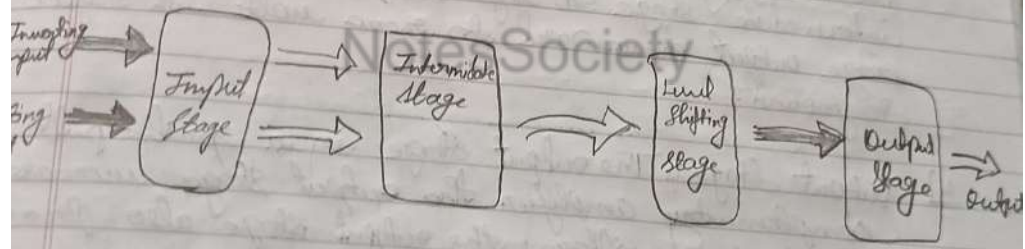

input stage is the dual input
differential amplifier. This stage
provides voltage gain and introduces the
operational amplifier.

This stage is a dual input
differential amplifier. This stage
provides voltage gain and introduces the
operational amplifier.

Since direct coupling is used
DC voltage the input of intermediate
ground potential hence the
for circuit is used after
shift the DC level at intermediate
and to zero volts with respect

input stage in a push-pull
for the output stage increase
the output stage also provides
vcc.

Characteristics of an ideal op-amp -

- 1] Open loop gain: Ideally op-amp should have an infinite open-loop gain (practically it is hundreds of thousand or times larger than the potential difference between its input terminals).
- 2] Input impedance or resistance: Ideally op-amp should have infinite input resistance (practically it should be very high).
- 3] Output: Output Impedance or resistance. Ideally op-amp should have zero output resistance (practically it should be very low).
- 4] Bandwidth: Ideally op-amp should have infinite bandwidth (practically it is limited).
- 5] CMRR: Ideally op-amp should have infinite CMRR, common mode rejection ratio. In the common mode noise voltage in the output becomes zero.
- 6] Slew rate: Ideally op-amp should have infinite SR, slew rate so that any change in the input voltage simultaneously change the output voltage.

Explain inverting amplifier and list characteristics of an ideal op-amp.

Ideal Op Amp.

- 1] An ideal op-amp exhibits the following characteristics




- 1] Input impedance $= Z_i = \infty \Omega$
2] Output Impedance $Z_o = 0 \Omega$
3] Open loop voltage gain $A_V = \infty$
4] If (The differential) input voltage $V_i = 0V$ then the output voltage will be $V_o = 0V$.

- 5] Bandwidth is infinity it means an ideal op-amp will amplify the signals of any frequency and attenuation

- 6] Common mode Rejection [CMRR] is infinity

Practical Op-Amp.

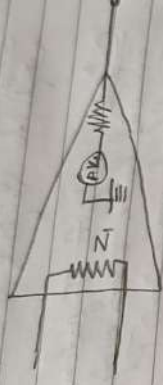Practically op-amp are not ideal and deviate from their ideal characteristics because of some imperfections. The practical op-amp is shown in the following figure.



A practical op-amp exhibits following characteristics:

Input impedance, Z_i in the order of mega ohms.

1] Input stage: - The input stage is the dual input balanced output differential amplifier. This stage provides most of the voltage gain and introduces an input resistance of operational amplifier.

2] Intermediate stage: This stage is a dual input unbalanced output differential amplifier which is biased by the output of the first stage.

3] Level shifting stage: Since direct coupling is used therefore the DC voltage the input of intermediate stage is above the ground potential hence the level shifting transistor circuit is used after intermediate stage to shift the DC level of intermediate stage output downward to zero volts with respect to ground.

4] Output stage: The output stage is a push-pull complementary amplifier the output stage increases the output voltage the output stage also provides low output resistance.

Ideal op

$$= V_i = V_o$$

$$\Rightarrow V_o/V_i = R_1 + R_f/R_i$$

$$\Rightarrow V_o/V_i = 1 + R_f/R_i$$

Non-Inverting amplifier


$$1 + R_f/R_i = V_o/V_i$$

Voltage Follower

→ A voltage follower is an electronic

→ Explain unity gain amplifier. ($A_v = 1$)

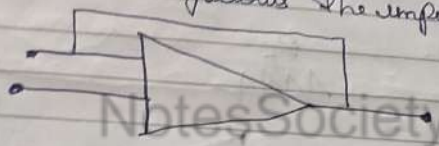→ A voltage follower is an electronic circuit which produces an output that follows the input voltage.



$$V_o = V_i$$

Application - Operational Amplifiers

- 1] Inverting and non-inverting adder.
- 2] Subtractor
- 3] Integrator
- 4] Differentiator
- 5] Logarithmic amplifier etc.

Nodal Equation at this terminal node is as show below.

$$i] (0 - v_i) / R_i + (0 - v_o) / R_f = 0$$

$$\Rightarrow -v_i / R_i = v_o / R_f$$

$$\Rightarrow v_o = (-R_f / R_i) v_i$$


$$\Rightarrow v_o / v_i = -R_f / R_i$$

Q Explain amplifier which have gain $av = -\frac{R_f}{R_i}$

→ The gain of inverting amplifier is equal to $-\frac{R_f}{R_i}$

Non-Inverting Amplifier.

i] A non-inverting

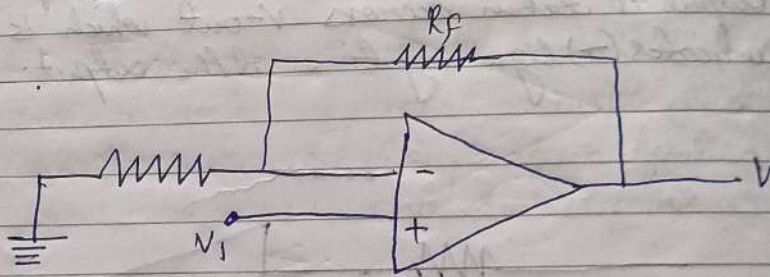

$$\Rightarrow v_i = v_o \left[\frac{R_i}{R_i + R_f} \right]$$

Basic application of operation amplifier

- 1] Inverting amplifier
- 2] Non-inverting amplifier
- 3] Voltage follower

Inverting amplifier

- 1] An inverting amplifier takes the input through its inverting terminal through a resistor, R_1 , and produces its amplified version as the output. This amplifier not only amplifies the input but also inverts it [changes its sign]

The \therefore

- 1] When input is applied to the inverting terminal

- 2] Non Inverting terminal is grounded
- 3] Feedback resistor is applied between input and output terminals. output is taken across V_{out} which is inverted output indicates (-) sign negative at the output.

